

Small modules

1. sign extend

a. code

```
1 module sign_extend( input  [15:0] sign_ex_in,  
2                       output reg [31:0] sign_ex_out);  
3  
4  
5     always@(sign_ex_in)  
6     begin  
7  
8         sign_ex_out = { {16{sign_ex_in[15]}}, sign_ex_in};  
9  
10    end  
11
```

b. TB

```
module sign_extend_tb;  
    reg [15:0] sign_ex_in;  
    wire [31:0] sign_ex_out;  
  
    sign_extend extension1 (sign_ex_in, sign_ex_out);  
  
    initial begin  
        $monitor("Time = %t | sign_ex_in = %b | sign_ex_out = %b", $time, sign_ex_in, sign_ex_out);  
  
        sign_ex_in = 16'b1010101010101010;  
        #10;  
        sign_ex_in = 16'b0101010101010101;  
        #10;  
        sign_ex_in = 16'b0000000000000000;  
        #10;  
        sign_ex_in = 16'b1111111111111111;  
        #10;  
        sign_ex_in = 16'b0000000011111111;  
        #10;  
        sign_ex_in = 16'b1111111110000000;  
    end  
    initial #100 $finish ;  
endmodule
```

c. RTL Viewer

sign_ex_in[15..0]  sign_ex_out[31..0]

d. Result

```
VSIM 3> run  
# Time = 0 | sign_ex_in = 1010101010101010 | sign_ex_out = 11111111111111110101010101010101  
# Time = 10 | sign_ex_in = 0101010101010101 | sign_ex_out = 00000000000000000101010101010101  
# Time = 20 | sign_ex_in = 0000000000000000 | sign_ex_out = 00000000000000000000000000000000  
# Time = 30 | sign_ex_in = 1111111111111111 | sign_ex_out = 11111111111111111111111111111111  
# Time = 40 | sign_ex_in = 0000000011111111 | sign_ex_out = 00000000000000000000000001111111  
# Time = 50 | sign_ex_in = 1111111100000000 | sign_ex_out = 1111111111111111111111111000000000
```

2. parameterized shift_left_twice

a. code

```
module shift_left_twice #(parameter width = 31)
  (input  [width:0] shift_in,
   output reg [31:0] shift_out);

  always @(shift_in)
  begin
    shift_out = shift_in << 2;
  end
endmodule
```

b. TB

1. when 32-bit input

```
module shift_left_twice_32_bit_tb;

  reg [31:0] shift_in;
  wire [31:0] shift_out;

  shift_left_twice #(.width(31)) shifter1
    (shift_in, shift_out);

  initial
  begin
    $monitor("time = %t | shift_in = %b | shift_out = %b", $time, shift_in, shift_out);
    shift_in = 32'b10101010101010101010101010101010;
    #10;
    shift_in = 32'b11111111111111111111111111111111;
    #10;
    shift_in = 32'b00000000000000000000000000000000;
    #10;
    shift_in = 32'b00000000000000001111111111111111;
  end

  initial #150 $finish;

endmodule
```

2. when 26-bit input

```
module shift_left_twice_26_bit_tb;

  reg [25:0] shift_in;
  wire [31:0] shift_out;


  shift_left_twice #(.width(25)) shifter1
    (shift_in, shift_out);

  initial
  begin
    $monitor("time = %t | shift_in = %b | shift_out = %b", $time, shift_in, shift_out);
    shift_in = 26'b101010101010101010101010101010;
    #10;
    shift_in = 26'b111111111111111111111111111111;
    #10;
    shift_in = 26'b000000000000000000000000000000;
    #10;
    shift_in = 26'b000000000000000011111111111111;
  end

  initial #150 $finish;

endmodule
```

c. RTL viewer

 

d. Result

```
# Loading work.shift_left_twice_26_bit_tb
# Loading work.shift_left_twice
VSIM 3> run
# time =          0 | shift_in = 10101010101010101010101010101010 | shift_out = 00001010101010101010101010101000
# time =         10 | shift_in = 11111111111111111111111111111111 | shift_out = 00001111111111111111111111111100
# time =         20 | shift_in = 00000000000000000000000000000000 | shift_out = 00000000000000000000000000000000
# time =         30 | shift_in = 00000000000000001111111111111111 | shift_out = 00000000000000000011111111111100
VSIM 4> vsim work.shift_left_twice_32_bit_tb
# vsim work.shift_left_twice_32_bit_tb
# Loading work.shift_left_twice_32_bit_tb
# Loading work.shift_left_twice
VSIM 5> run
# time =          0 | shift_in = 10101010101010101010101010101010 | shift_out = 10101010101010101010101010101000
# time =         10 | shift_in = 11111111111111111111111111111111 | shift_out = 11111111111111111111111111111100
# time =         20 | shift_in = 00000000000000000000000000000000 | shift_out = 00000000000000000000000000000000
# time =         30 | shift_in = 00000000000000000011111111111111 | shift_out = 00000000000000000011111111111100
```

3.adder


a. code

```
1 module adder( input [31:0] data_in1, data_in2,  
2               output [31:0] result);  
3  
4   assign result = data_in1 + data_in2;  
5  
6   endmodule  
7
```

b. TB

```
8  
9 module adder_tb;  
10  
11   reg [31:0] data_in1, data_in2;  
12   wire [31:0] result;  
13  
14   adder add1 (data_in1, data_in2, result);  
15  
16   initial  
17   begin  
18     $monitor("time = %t | data_in1 = %d | data_in2 = %d | result = %d ",$time, data_in1, data_in2, result);  
19     // $monitor("time = %t | data_in1 = %b | data_in2 = %b | result = %b ",$time, data_in1, data_in2, result);  
20  
21     data_in1 = 10;  
22     data_in2 = 5;  
23     #10;  
24  
25     data_in1 = 16;  
26     data_in2 = 4;  
27     #10;  
28  
29     data_in1 = 30;  
30     data_in2 = 10;  
31     #10;  
32  
33     data_in1 = 32;  
34     data_in2 = 8;  
35   end  
36  
37   initial #150 $finish;  
38  
39 endmodule
```

c. RTL Viewer

 

d. Result

```
VSIM 4> run  
# time = 0 | data_in1 = 10 | data_in2 = 5 | result = 15  
# time = 10 | data_in1 = 16 | data_in2 = 4 | result = 20  
# time = 20 | data_in1 = 30 | data_in2 = 10 | result = 40  
# time = 30 | data_in1 = 32 | data_in2 = 8 | result = 40
```

 

2. 32-bit in/out

```
//32-bit mux
module mux2_1_tb32;
reg [31 : 0] in1, in2;
reg sel;
wire [31 : 0] out_mux;

mux2_1 #(31) muxtest ( in1, in2, sel, out_mux);

initial
begin
    $monitor("time = %t | in1 = %b | in2 = %b | sel = %b | out_mux = %b", $time, in1, in2, sel, out_mux);
    in1 = {32{1'b1}};
    in2 = 32'b0;
    sel = 1'b0;
    #10
    in1 = {32{1'b1}};
    in2 = 32'b0;
    sel = 1'b1;
end
initial #150 $finish;
endmodule
```

c. RTL Viewer



d. Result

```
VSIM 3> run
# time =          0 | in1 = 11111 | in2 = 00000 | sel = 0 | out_mux = 11111
# time =         10 | in1 = 11111 | in2 = 00000 | sel = 1 | out_mux = 00000
VSIM 4> vsim work.mux2_1_tb32
# vsim work.mux2_1_tb32
# Loading work.mux2_1_tb32
# Loading work.mux2_1
VSIM 5> run
# time =          0 | in1 = 11111111111111111111111111111111 | in2 = 00000000000000000000000000000000 | sel = 0 | out_mux = 11111111111111111111111111111111
# time =         10 | in1 = 11111111111111111111111111111111 | in2 = 00000000000000000000000000000000 | sel = 1 | out_mux = 00000000000000000000000000000000
```

Main modules

1. Alu

a. Code

```
module Alu(input [31:0] scr_A, scr_B,
           input [2:0] alu_ctr,
           output reg [31:0] result,
           output reg z_flag );

    always @(*)
    begin
        result='b0;
        z_flag='b1;
        case(alu_ctr)
            //bitwise and
            3'b000: begin
                result = scr_A & scr_B;
                if(result == 0) begin
                    z_flag = 1;
                end else begin
                    z_flag = 0;
                end
            end
            //bitwise or
            3'b001: begin
                result = scr_A | scr_B;
                if(result == 0) begin
                    z_flag = 1;
                end else begin
                    z_flag = 0;
                end
            end
            //addition
            3'b010: begin
                result = scr_A + scr_B;
                if(result == 0) begin
                    z_flag = 1;
                end else begin
                    z_flag = 0;
                end
            end
            //subtraction
            3'b100: begin
                result = scr_A - scr_B;
                if(result == 0) begin
                    z_flag = 1;
                end else begin
                    z_flag = 0;
                end
            end
            //multiplication
            3'b101: begin
                result = scr_A * scr_B;
                if(result == 0) begin
                    z_flag = 1;
                end else begin
                    z_flag = 0;
                end
            end
        endcase
    end
end
```

```

//set less than (if srca < srcb then aluresult = 1 )
3'b110: begin
if(scr_A < scr_B) begin
    result = 1;
end else begin
    result = 0;
end
if(result == 0) begin
    z_flag = 1;
end else begin
    z_flag = 0;
end
end

default : begin
    result = 0;
    z_flag = 1'b1;
end

endcase
end
endmodule

```

b. Alu TB

```

module Alu_tb;

reg [31:0] scr_A, scr_B;
reg [2:0] alu_ctr;
wire [31:0] result;
wire z_flag;

Alu Alu_test(scr_A, scr_B, alu_ctr, result, z_flag);
initial
begin
    $monitor("time = %t | scr_A = %b | scr_B = %b | alu_ctr = %b | result = %b | z_flag = %b", $time, scr_A, scr_B, alu_ctr, result, z_flag);
    // test all cases for alu_ctr when (scr_a > scr_B)
    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b000;
    #10;

    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b001;
    #10;

    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b010;
    #10;

    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b011;
    #10;

    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b100;
    #10;

    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b101;
    #10;

    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b110;
    #10;

    scr_A = 15;
    scr_B = 10;
    alu_ctr = 3'b111;
    #10;
end
endmodule

```



```

//-----//
// test all cases for alu_ctr when (scr_a < scr-B)
scr_A = 15;
scr_B = 20;
alu_ctr = 3'b000;
#10;

scr_A = 15;
scr_B = 20;
alu_ctr = 3'b001;
#10;

scr_A = 15;
scr_B = 20;
alu_ctr = 3'b010;
#10;

scr_A = 15;
scr_B = 20;
alu_ctr = 3'b011;
#10;

scr_A = 15;
scr_B = 20;
alu_ctr = 3'b100;
#10;

scr_A = 15;
scr_B = 20;
alu_ctr = 3'b101;
#10;

scr_A = 15;
scr_B = 20;
alu_ctr = 3'b110;
#10;

scr_A = 15;
scr_B = 20;
alu_ctr = 3'b111;
#10;

```

```

//-----//
// test all cases for alu_ctr when (scr_a = scr-B)
scr_A = 10;
scr_B = 10;
alu_ctr = 3'b000;
#10;

scr_A = 10;
scr_B = 10;
alu_ctr = 3'b001;
#10;

scr_A = 10;
scr_B = 10;
alu_ctr = 3'b010;
#10;

scr_A = 10;
scr_B = 10;
alu_ctr = 3'b011;
#10;

scr_A = 10;
scr_B = 10;
alu_ctr = 3'b100;
#10;

scr_A = 10;
scr_B = 10;
alu_ctr = 3'b101;
#10;

scr_A = 10;
scr_B = 10;
alu_ctr = 3'b110;
#10;

scr_A = 10;
scr_B = 10;
alu_ctr = 3'b111;
#10;

end

initial #250 $finish;
endmodule

```

c. Result

1. for first case of testing

	Msgs								
/Alu_tb/scr_A	10	15							
/Alu_tb/scr_B	10	10							
/Alu_tb/alu_ctr	101	000	001	010	011	100	101	110	111
/Alu_tb/result	100	10	15	25	0	5	150	0	
/Alu_tb/z_flag	St0								

2. 2nd case

	Msgs								
/Alu_tb/scr_A	10	15							
/Alu_tb/scr_B	10	20							
/Alu_tb/alu_ctr	101	000	001	010	011	100	101	110	111
/Alu_tb/result	100	4	31	35	0	-5	300	1	0
/Alu_tb/z_flag	St0								

3. 3rd case of testing

10							
10							
000	001	010	011	100	101	110	111
10		20	0		100	0	

2. Program Counter

a. Code

```
1 module pc(input [31:0] pc_in, // the output of the instruction memory in case of jump & branch
2           input clk, n_rst,
3           input jump, pcsrc, //control signals to detect branch and jump case
4           output reg [31:0] pc_out);
5 wire [31:0] pcplus4 = pc_out + 4;
6 wire [31:0] sn_ex_temp;
7 sign_extend ex (pc_in[15:0], sn_ex_temp);
8 always@(posedge clk or negedge n_rst)
9 begin
10     if(!n_rst) begin
11         pc_out <= 32'b0;
12     end else begin
13         case({jump, pcsrc})
14             2'b00: pc_out <= pcplus4 ;
15             2'b01: pc_out <= pcplus4 + (sn_ex_temp << 2);
16             2'b10: pc_out <= {pcplus4[31:28],pc_in[25:0],2'b00};
17             default: pc_out <= pcplus4 ;
18         endcase
19     end
20 end
21 endmodule
```

b. TB

1. case #1 (Reset)

```
38 module pc_tb;
39 reg [31:0] pc_in; // instruction
40 reg clk, n_rst;
41 reg jump, pcsrc;
42 wire [31:0] pc_out;
43 pc pc_test(pc_in, clk, n_rst, jump, pcsrc, pc_out);
44 // Clock generation
45 always #5 clk = ~ clk;
46 initial begin
47     // Test case 1: n_rst is low, output is expected to be cleared (pc_out = 0)
48     clk = 0;
49     n_rst = 1'b0; // Assert reset
50     #10;
51     if (pc_out !== 32'b0)
52         $display("Test case 1 failed: pc_out= %b ", pc_out);
53     else
54         $display("Test case 1 passed");
55 end
```

2. case#2 (R-type) to increase PC by 4

```
61 // Test case 2:n_rst is high & R-type instruction
62 jump = 0; // No jump
63 psrc = 0; // No branch
64 pc_in = 32'b0000001000110010100000000100000; // add $s0, $s1, $s2
65 n_rst = 1; // Release reset
66 #10;
67
68 if (pc_out !== 4)
69     $display("Test case 2 failed: pc_out = %b ", pc_out);
70 else
71     $display("Test case 2 passed");
72
```

3. case#3 (j-type) to make PC jump to address 1028(decimal)

```
73 // Test case 3:n_rst is high and there is jump instruction
74 jump = 1; // jump
75 psrc = 0; // No branch
76 pc_in = 32'b00001000000000000000000100000001; // j 1028
77 n_rst = 1; // Release reset
78
79 #10;
80
81 if (pc_out !== 1028)
82     $display("Test case 2 failed: pc_out = %b | pc_out<decimal> = %d", pc_out, pc_out);
83 else
84     $display("Test case 2 passed");
85
```

4. case#4 (beq) to make PC branch at a label at address 1048(decimal)

```
81 if (pc_out !== 1028)
82     $display("Test case 2 failed: pc_out = %b | pc_out<decimal> = %d", pc_out, pc_out);
83 else
84     $display("Test case 2 passed");
85
86 // Test case 4:n_rst is high and there is branch instruction
87
88 jump = 0; // No jump
89 psrc = 1; // branch
90 pc_in = 32'b0001000100000000000000000000100; // beq at a label at 1048
91 n_rst = 1; // Release reset
92
93 #10;
94
95 if (pc_out !== 1048)
96     $display("Test case 2 failed: pc_out = %b | pc_out<decimal> = %d", pc_out, pc_out);
97 else
98     $display("Test case 2 passed");
99
```


5. case#5 assert the reset to make PC go back to address 0

```
99
100 // Test case 5: n_rst is low, output is expected to be cleared (pc_out = 0)
101 n_rst = 1'b0; // Assert reset
102 #10;
103
104 if (pc_out !== 32'b0)
105     $display("Test case 1 failed: pc_out= %b ", pc_out);
106 else
107     $display("Test case 1 passed");
108
109
110 end
111 initial #1000 $finish;
112 endmodule
```

b. Results

```
# Test case 1 passed
# Test case 2 passed
# Test case 3 passed
# Test case 4 passed
# Test case 5 passed
```

Waves:

 

3. Instruction memory

a. code

```
1 module inst_mem(input [31:0] address,
2                 output reg[31:0] instruction);
3
4   reg [31:0] inst_array [255:0];
5
6   initial $readmemh("programone.hex",inst_array);
7
8   always @(*)
9   begin
10    instruction = inst_array[address[9:2]];
11  end
12 endmodule
13
```

Programone.hex is a hexadecimal file containing the following machine code

1- Number Factorial: (hex format)


```
00008020
20100007    // change the least two significant decimals with the number
00008820
20110001
12000003
0230881C
2210FFFF
08000004
AC110000
```

b. TB

```
15
16 module tb;
17 reg [31:0] address;
18 wire [31:0] instruction;
19
20 inst_mem test1(address, instruction);
21
22 initial
23 begin
24     $monitor("time = %t | address = %d | instruction = %h", $time, address, instruction);
25     address = 0;
26     #10
27     address = 4;
28     #10
29     address = 8;
30     #10
31     address = 12;
32     #10
33     address = 16;
34     #10
35     address = 20;
36     #10
37     address = 24;
38     #10
39     address = 28;
40     #10
41     address = 32;
42     end
43
44 initial #150 $finish;
45 endmodule
46
```

c. Results

```
# time =          0 | address =          0 | instruction = 00008020
# time =         10 | address =          4 | instruction = 20100007
# time =         20 | address =          8 | instruction = 00008820
# time =         30 | address =         12 | instruction = 20110001
# time =         40 | address =         16 | instruction = 12000003
# time =         50 | address =         20 | instruction = 0230881c
# time =         60 | address =         24 | instruction = 2210ffff
# time =         70 | address =         28 | instruction = 08000004
# time =         80 | address =         32 | instruction = ac110000
```

 

4. Register file

a. Code

```

1 module Register_file(input [4:0] r_a1, r_a2,           // READ ADDRESSES
2                       input [4:0] w_a3,               // WRITE ADDRESS
3                       input [31:0] w_d,               // WRITE DATA
4                       input w_e3, clk,               // WRITE ENABLE & CLK
5                       output [31:0] r_d1, r_d2);      // READ DATA
6
7     reg [31:0] registers [31:0];
8
9     integer i;
10    initial begin
11        for(i = 0; i < 32; i = i + 1) begin
12            registers[i] = 32'b0;
13        end
14    end
15
16    // asynchronus data reading
17    assign r_d1 = registers[r_a1];
18    assign r_d2 = registers[r_a2];
19
20    // synchronus data writing
21    always @(posedge clk)
22    begin
23        if(w_e3) begin
24            if(w_a3 != 0) registers[w_a3] <= w_d ; // as register zero is always zero
25        end else begin
26            registers[w_a3] <= registers[w_a3];
27        end
28    end
29
30 endmodule
31
32
33
34

```

b. TB

```

44 module r_f_TB;
45 reg [4:0] r_a1, r_a2, w_a3;
46 reg [31:0] w_d;
47 reg w_e3, clk;
48 wire[31:0] r_d1, r_d2;
49
50 Register_file m(r_a1, r_a2, w_a3, w_d, w_e3, clk, r_d1, r_d2);
51 always #10 clk = ~ clk;
52 initial begin
53     $monitor("time = %t | read_address_1 = %d | read_address_2 = %d | write_address = %d | written_data = %h | enable = %b | read_
54     clk = 0;
55     r_a1 = 7;
56     r_a2 = 3;
57     w_e3 = 0;
58     w_a3 = 1;
59     #20
60
61     w_e3 = 1;
62     w_a3 = 1;
63     w_d = 32'b001000010000000000000000011001010;
64     #20
65
66     w_e3 = 0;
67     w_d = 0;
68     r_a1 = 1;
69     r_a2 = 0;
70
71 end
72
73 initial #2000 $finish;
74 endmodule
75
76


```

c. Result (same as expected)

```

|add wave -position insertpoint sim:/r_f_TB/
VSI4> run
# time =          0 | read_address_1 = 7 | read_address_2 = 3 | write_address = 1 | written_data = xxxxxxxx | enable = 0 | read_data_1 = 00000000 | read_data_2 = 00000000
# time =         20 | read_address_1 = 7 | read_address_2 = 3 | write_address = 1 | written_data = 210000ca | enable = 1 | read_data_1 = 00000000 | read_data_2 = 00000000
# time =         40 | read_address_1 = 1 | read_address_2 = 0 | write_address = 1 | written_data = 00000000 | enable = 0 | read_data_1 = 210000ca | read_data_2 = 00000000

```

 

5. Data Memory

a. Code

```
1
2 module data_mem(input [31:0] addr, w_d,
3                 input clk, w_e,
4                 output reg[31:0] r_d,
5                 output [15:0] test_value);
6
7     reg [31:0] data_array [255:0];
8
9     integer i;
10    initial begin
11        r_d = 32'b0;
12        for(i = 0; i < 256; i = i + 1) begin
13            data_array[i] = 32'b0;
14        end
15    end
16
17    always @ (posedge clk)
18    begin
19        if(w_e) begin
20            data_array[addr[9:2]] <= w_d;
21        end else begin
22            data_array[addr[9:2]] <= data_array[addr[9:2]];
23        end
24    end
25
26    always @(*)
27    begin
28        if(~w_e) begin
29            r_d <= data_array[addr[9:2]];
30        end else begin
31            r_d <= r_d;
32        end
33    end
34
35    assign test_value = r_d[15:0];
36
37 endmodule
```

b. TB


```
37
38 module d_m_TB;
39     reg [31:0] w_d, addr;
40     reg        w_e, clk;
41     wire[31:0] r_d;
42     wire [15:0] test_value;
43
44     data_mem d (addr, w_d, clk, w_e, r_d, test_value);
45     always #10 clk = ~ clk;
46
47     initial begin
48         $monitor("time=%t | address = %d | enable = %b | written_data = %h | read_data = %h");
49         clk = 0;
50         addr = 5;
51         w_e = 0;
52         w_d = 32'b00000000000000000001001000110100;
53         #20
54         w_e = 1;
55         #20
56         w_e = 0;
57
58         end
59
60     initial #2000 $finish;
61
62 endmodule
```

c. Result (same as expected)

```

VSIM 3> run
# time=      0 | address =      5 | enable = 0 | written_data = 00001234 | read_data = 00000000 | test_value = 0000
# time=     20 | address =      5 | enable = 1 | written_data = 00001234 | read_data = 00000000 | test_value = 0000
# time=     40 | address =      5 | enable = 0 | written_data = 00001234 | read_data = 00001234 | test_value = 1234

```

 

6. Control unit (which is divided into main decoder and Alu decoder)

a. Top module code

```

1 module ctrl_unit (input  [5:0] op_code, funct,
2                   output jump, memwrite, regwrite, redest, alusrc, memtoreg, branch,
3                   output  [2:0] alu_ctrl);
4
5   wire [1:0] alu_op;
6   main_decoder d1(op_code, jump, memwrite, regwrite, redest, alusrc, memtoreg, branch, alu_op);
7   alu_decoder  d2(alu_op, funct, alu_ctrl);
8 endmodule
9

```

b. main decoder code

```
11 module main_decoder (input [5:0] op_code,  
12                      output reg jump, memwrite, regwrite, redest, alusrc, memtoreg, branch,  
13                      output reg [1:0] alu_op);  
14 always @(*) begin  
15     case(op_code)  
16     6'b100011: begin  
17         jump = 0;  
18         alu_op = 0;  
19         memwrite = 0;  
20         regwrite = 1'b1;  
21         redest = 0;  
22         alusrc = 1'b1;  
23         memtoreg = 1'b1;  
24         branch = 0;  
25     end  
26     6'b101011: begin  
27         jump = 0;  
28         alu_op = 0;  
29         memwrite = 1'b1;  
30         regwrite = 0;  
31         redest = 0;  
32         alusrc = 1'b1;  
33         memtoreg = 1'b1;  
34         branch = 0;  
35     end  
36     6'b000000: begin  
37         jump = 0;  
38         alu_op = 2'b10;  
39         memwrite = 0;  
40         regwrite = 1'b1;  
41         redest = 1'b1;  
42         alusrc = 0;  
43         memtoreg = 0;  
44         branch = 0;  
45     end  
46     6'b001000: begin  
47         jump = 0;  
48         alu_op = 0;  
49         memwrite = 0;  
50         regwrite = 1'b1;  
51         redest = 0;  
52         alusrc = 1'b1;  
53         memtoreg = 0;  
54         branch = 0;  
55     end  
56     6'b000100: begin  
57         jump = 0;  
58         alu_op = 2'b01;  
59         memwrite = 0;  
60         regwrite = 0;  
61         redest = 0;  
62         alusrc = 0;  
63         memtoreg = 0;  
64         branch = 1'b1;  
65     end  
66     6'b000010: begin  
67         jump = 1'b1;  
68         alu_op = 0;  
69         memwrite = 0;  
70         regwrite = 0;  
71         redest = 0;  
72         alusrc = 0;  
73         memtoreg = 0;  
74         branch = 0;  
75     end  
76     default: begin  
77         jump = 0;  
78         alu_op = 0;  
79         memwrite = 0;  
80         regwrite = 0;  
81         redest = 0;  
82         alusrc = 0;  
83         memtoreg = 0;  
84         branch = 0;  
85     end  
86 endcase  
87 end  
88 endmodule
```


c. Alu Decoder

```

96
97 module alu_decoder(input  [1:0] alu_op,
98                     input  [5:0] funct,
99                     output reg [2:0] alu_ctrl);
100
101 always @(*)
102 begin
103     case(alu_op)
104         2'b00: alu_ctrl = 3'b010;
105         2'b01: alu_ctrl = 3'b100;
106         2'b10: begin
107             case(funct)
108                 6'b100000: alu_ctrl = 3'b010;
109                 6'b100010: alu_ctrl = 3'b100;
110                 6'b101010: alu_ctrl = 3'b110;
111                 6'b011100: alu_ctrl = 3'b101;
112                 default : alu_ctrl = 3'b010;
113             endcase
114         end
115         default: alu_ctrl = 3'b010;
116     endcase
117 end
118 endmodule

```

d. RTL viewer

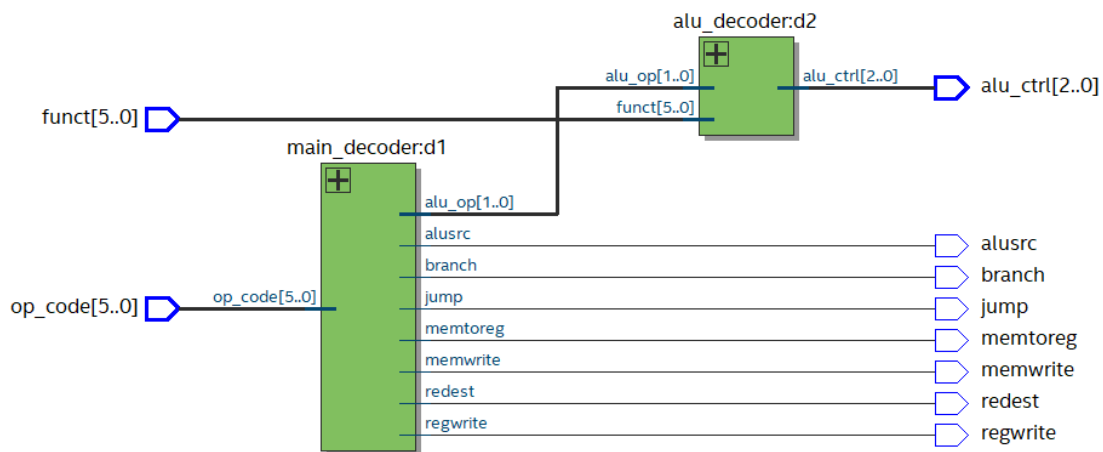

e. TB

```

130 module ctrl_unit_TB;
131
132 reg [5:0] op_code, funct;
133 wire jump, memwrite, regwrite, redest, alusrc, memtoreg, branch;
134 wire [2:0] alu_ctrl;
135
136 ctrl_unit b (op_code, funct, jump, memwrite, regwrite, redest, alusrc, memtoreg,
137
138 initial begin
139     $monitor("time=%t| op_code = %b | funct = %b | jump = %b| memwrite = %b| regwrite
140
141     op_code = 6'b100011;
142     funct    = 6'b011100;
143     #20
144
145     op_code = 6'b000000;
146     funct    = 6'b011100;
147
148 end
149
150 initial #2000 $finish;
151
152 endmodule

```

f. Results (same as expected)


```
# -- Compiling module alu_decoder
# -- Compiling module ctrl_unit_TB
#
# Top level modules:
#     ctrl_unit_TB
#
#ModelSim> vsim work.ctrl_unit_TB
# vsim work.ctrl_unit_TB
# Loading work.ctrl_unit_TB
# Loading work.ctrl_unit
# Loading work.main_decoder
# Loading work.alu_decoder
add wave -position insertpoint sim:/ctrl_unit_TB/*
/SIM 4> run
# time=          0| op_code = 100011 | funct = 011100 | jump = 0| memwrite = 0| regwrite = 1 | redest= 0| alusrc= 1| memtoreg= 1| branch = 0| alu_ctrl = 010
# time=         20| op_code = 000000 | funct = 011100 | jump = 0| memwrite = 0| regwrite = 1 | redest= 1| alusrc= 0| memtoreg= 0| branch = 0| alu_ctrl = 101
/SIM 5>
```

	Msgs								
+ /ctrl_unit_TB/op_code	000000	100011	000000						
+ /ctrl_unit_TB/funct	011100	011100							
/ctrl_unit_TB/jump	St0								
/ctrl_unit_TB/memwrite	St0								
/ctrl_unit_TB/regwrite	St1								
/ctrl_unit_TB/redest	St1								
/ctrl_unit_TB/alusrc	St0								
/ctrl_unit_TB/memtoereg	St0								
/ctrl_unit_TB/branch	St0								
+ /ctrl_unit_TB/alu_ctrl	101	010	101						

Top module for single cycle MIPS processor

Using all of the previous blocks (sub-modules)

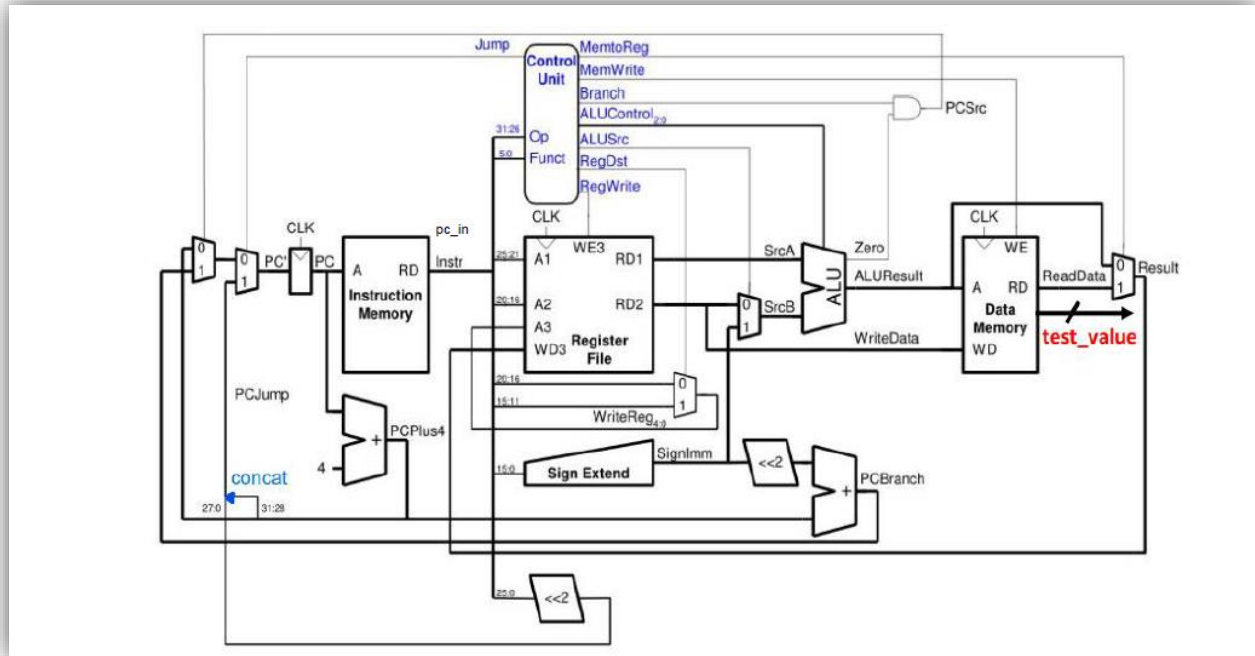- According to the following connection between the pre-designed modules, the top-level module is designed as explained in the following code.



a. Code

```

1 module MIPS(input clk, reset,
2             output [15:0] test_value);
3
4 wire        jump, memwrite, regwrite, redest, alusrc, memtoreg, branch, pcsrc, z_flag;
5 wire [4:0]   writereg;
6 wire [2:0]   alu_ctrl;
7 wire [31:0] alu_result, pr_c, inst, readdata, signimm, scr_B, r_d1, r_d2, result;
8
9 ctrl_unit    m1 (inst[31:26], inst[5:0], jump, memwrite, regwrite, redest, alusrc, memtoreg,
10 mux2_1 #(4)  m2 (inst[20:16], inst[15:11], redest, writereg);
11 Register_file m3 (inst[25:21], inst[20:16], writereg, result, regwrite, clk, r_d1, r_d2);
12 sign_extend  m4 (inst[15:0], signimm);
13 mux2_1 #(31) m5 (r_d2, signimm, alusrc, scr_B);
14 Alu          m6 (r_d1, scr_B, alu_ctrl, alu_result, z_flag);
15 data_mem     m7 (alu_result, r_d2, clk, memwrite, readdata, test_value);
16 mux2_1 #(31) m8 (alu_result, readdata, memtoreg, result);
17 assign pcsrc = z_flag & branch;
18 pc           m9 (inst, clk, reset, jump, pcsrc, pr_c);
19 inst_mem     m10 (pr_c, inst);
20
21 endmodule

```


b. TB

```

23
24 module MIPS_TB;
25 reg clk, reset;
26 wire [15:0]test_value;
27
28 MIPS mm (clk, reset, test_value);
29 always #10 clk = ~ clk;
30
31 initial begin
32     $monitor("time = %t | reset = %b | test_value = %h ",$time, reset, test_value);
33
34     clk = 0;
35     reset = 1'b0;
36     #20;
37     reset = 1'b1;
38
39     end
40 endmodule
41
42

```

c. Results (7 factorial)

 

d. Results (CGD)

